

2201-COL215 Major exam

Aaveg Jain

TOTAL POINTS

99.5 / 120

QUESTION 1

Boolean postulates 15 pts

1.1 Part a 5 / 6

- ✓ + 1 pts Closure is satisfied (1 is in {0,1})
 - + 1 pts Commutativity is satisfied (both operands are equal)
- ✓ + 1 pts Inverse can be satisfied (if we define 1 as the inverse of 0, and 1 AND 0 = 0)
- ✓ + 1 pts Multiplicative identity is not relevant (since it applies only when an operand is '1')
 - + 0 pts Distributivity is ignored. As it was mentioned in paper to ignore hence no credit
- ✓ + 2 pts Correct answer: Yes
 - + 0 pts Incorrect
 - please write neatly

1.2 Part b 7.5 / 9

- ✓ + 3 pts Assignment satisfies identity rules
 - 1.5 pts Justification not given for identity rules
- ✓ + 3 pts Assignment satisfies commutativity rules
 - 1.5 pts Justification not given for commutativity rules
- + 3 pts U' defined correctly
- ✓ + 1.5 pts U' not explicitly written but inverse postulate considered
 - + 0 pts Incorrect

QUESTION 2

2 D flipflop synchronous reset 10 / 10

- ✓ + 5 pts Identify the correct signals (input and reset complement)
 - ✓ + 5 pts Used AND gate to feed the input of D flip flop
 - + 7 pts Used another flip flop for reset (only circuit), this will cost more area and timing delay will be more before reset occurs
- + 0 pts incorrect/not attempted
- + 0 pts No justification

QUESTION 3

Hamming code 10 pts

- 3.1 Flip the bit 5 / 5
- ✓ + 2 pts Correct Answer
 - ✓ + 3 pts Explanation
 - + 0 pts Incorrect

3.2 Parity and data bits 5 / 5

- ✓ + 5 pts Correct
- + 0 pts Incorrect
- ✓ + 0 pts Justification

QUESTION 4

4 3x8 decoder 10 / 10

- + 0 pts Not Answered.
- ✓ + 5 pts connecting two decoders.

✓ + 5 pts *Correct final output.*

QUESTION 5

5 Magnitude comparator 10 / 10

✓ + 10 pts *Correct*

+ 0 pts Incorrect/not attempted

+ 5 pts Partial (didn't explain which term generation is not possible via xor)

QUESTION 6

6 DRAM address sequence 0 / 10

✓ + 0 pts *InCorrect*

+ 5 pts Mentioned Increasing or Decreasing order

+ 5 pts Justification is given

QUESTION 7

7 Representation of netlist 5 / 10

✓ + 2 pts *Appropriate data structure identified (as graph)*

✓ + 2 pts *Representation of gates (as node in graph)*

✓ + 2 pts *Attribute to represent functionality of gate (enum {AND,OR, INV etc}, truth table or boolean expression)*

✓ + 2 pts *Connections between gates (as edge in graph)*

✓ + 2 pts *primary inputs and output representation (as node in graph)*

+ 0 pts Incorrect/not attempted

- 5 Point adjustment

☞ input as leave will not work for the netlist. As in tree there can be only one path from parent node to leaf but in netlist multiple paths are possible

QUESTION 8

8 VHDL concurrent statements 9 / 10

✓ + 4 pts *Identification of dependency*

✓ + 3 pts *Correct Order of Execution*

+ 1 pts Manage Execution Status

✓ + 2 pts *Example Given*

+ 0 pts Incorrect/Not Answered

QUESTION 9

9 FSM symbolic states 10 / 10

✓ + 7 pts *Symbolic states can be used to represent any state/assignment encoding. Some encodings may lead to better circuit than others.*

✓ + 3 pts *Starting with 00/01 fixes the encoding at the specification itself. (Limitation)*

+ 5 pts Partially Correct / Correct Idea

+ 0 pts Incorrect/Not Attempted

QUESTION 10

10 State reduction 9 / 10

✓ + 4 pts *State reduction reduces the size of the netlist. - no*

✓ + 4 pts *Correct explanation*

✓ + 1 pts *Correct sequential logic example*

+ 1 pts *Correct combination logic example*

+ 0 pts *Incorrect/Unattempted*

QUESTION 11

11 Overlapping wires 14 / 15

✓ + 12 pts *Correctly drawn circuit without directly using XOR gate*

✓ + 3 pts *Correctly marked signals in circuit or correctly explained the changes in signals*

+ 0 pts *Incorrect/ used non-allowed*

gate/overlapping wires/ Wire crossings

- 1 Point adjustment

- Not explained how NAND forms XOR.

Department of Computer Science and Engineering, IIT Delhi

Digital Logic and System Design (COL 215)

I Semester 2022-23

Major Exam

Maximum Marks: 120

17 November 2022, 11:00 AM to 1:00 PM

Answer ONLY in the spaces indicated below the questions. Answers written elsewhere will be ignored.

1. [6+9 = 15 Marks]

- a. [6 Marks] Suppose we propose an algebra in which **0 AND 0** is defined to be **1**. Does this proposal satisfy the postulates of Boolean algebra we studied in class? Justify. [Ignore the postulates that involve **OR**, as we haven't defined the **OR** operation.]

(algebra has 2 values {0,1}).

Yes; the postulates involving AND only are
 and comm. of AND
 $x \cdot 1 = x$; $x \cdot \bar{x} = 0$ if $x = 0$, then we have $0 \text{ AND } 0 = 1$
 from second postulate, observe \bar{x} cannot be 0 as $0 \text{ AND } 0 = 1 \neq 0$
 thus set $\bar{x} = 1$ and $0 \text{ AND } \bar{0} = 0$ and $1 = 0$; this does not violate the first postulate as $0 \cdot \bar{x} = 0$ and $1 = 0$
 thus, it satisfies the postulates. (comm. is also satisfied)

- b. [9 Marks] Suppose we define an algebra with **THREE** values **{0,1,U}**, (where **U** could represent, for example, the *Uninitialised* state of a signal...although that is not important for this question). Fill in the following table to define the **AND** operation with values that are consistent with the postulates of Boolean algebra. Justify your answers. [Fill in the value of **X AND Y** in the row corresponding to **X** and column corresponding to **Y**. Ignore the postulates that involve **OR**, as we haven't defined the **OR** operation.]

	0	1	U
0	0	0	0
1	0	1	U
U	0	U	0

the relevant postulates are

$$\textcircled{1} x \cdot 1 = x \text{ and } \textcircled{2} x \cdot \bar{x} = 0, \textcircled{3} \text{ of AND}$$

~~=> x · 1 = x, x · 0 = 0~~

define complement as foll-

$$\bar{U} = U, \bar{0} = 1, \bar{1} = 0$$

for row 01, we have $U \cdot 1 = U, 0 \cdot 1 = 0, 1 \cdot 1 = 1$

(from first post.)

also, from second postulate

$$U \cdot \bar{U} = U \cdot U = 0, 1 \cdot \bar{1} = 1 \cdot 0 = 0, 0 \cdot \bar{0} = 0 \cdot 1 = 0$$

let $0 \cdot 0 = 0$ and $U \cdot 0 = 0$ to obtain the given table. also, it is observed that commutativity is satisfied in all cases.

$$\begin{matrix} R & D & D' \\ 0 & 1 & 1 \\ D & 0 & 0 \\ 1 & 0 & 0 \\ 1 & 1 & 0 \end{matrix}$$

$$D = R'D + R B$$

$$R'D = D$$

$$\begin{matrix} R & D & D' \\ 0 & 0 & 0 \\ 1 & 0 & 0 \end{matrix} \quad D' = RD \text{ term} = R^k D$$

$$k=2^{n-1} \quad n+k \geq 2^{k-1}$$

$$n \geq 4 \quad n=5$$

$$q_{r,n} \quad k=3 \quad n=5$$

$$\begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 & 8 \\ P_1 & P_2 & 0 & P_3 & 1 & 0 & 1 & 0 \\ =0 & =0 & & =0 & & & & \end{matrix}$$

~~resolveremos~~

$$0 \ 1 \ 0 \ 0 \ 1 \ 0 \ 1 \ 0$$


$$\begin{array}{r} 001 \\ 010 \\ 011 \\ 0100 \\ 101 \\ 110 \\ 111 \\ \hline 0+ \\ 60 \\ \hline P_3 = 1 \end{array}$$

111

111

$$\begin{matrix} 0 & \oplus & 1 \\ 3 & 6 & 7 \end{matrix}$$

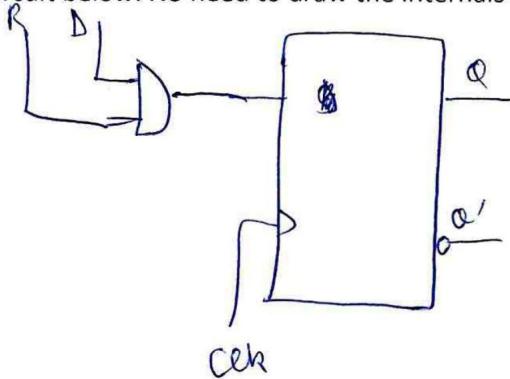2. [10 Marks] We have studied the design of a D flip-flop with an asynchronous reset, where the reset signal works independently of the clock. Design a variation of the D flip-flop with a **synchronous reset**. In this design, the reset signal does not act independently of the clock; instead, the reset signal influences the Q value only at the rising edge of the clock. Draw the circuit below. No need to draw the internals of the D flip-flop.



R is the Reset signal and is active low

(we introduce a new input signal R)

3. [5+5 = 10 Marks] In the error correction mechanism using *Hamming Code*, where **k** parity bits are added to an **n**-bit data word, the error is corrected by flipping the bit corresponding to the **C** outputs.

- a. [5 Marks] If the **C** outputs do not point to a data bit, is it still right to flip the bit? Why?




Yes, if it doesn't point to a data bit, then also we should flip the corr. parity bit. If **C** points to a parity bit, it means that during read the parity bit got flipped. When we find **C**, we take XOR of all data bits with **C** at positions along with corr. parity bit also. Then, if a parity bit flips, then the corr. parity bit position is reflected in **C**.

- b. [5 Marks] What relationship must be satisfied between **n** and **k**, for the error correction to work properly? (**C** is of **k** bits (**k** parity bits)


thus range of values it can represent is $0 \text{ to } 2^k - 1$. assuming 0 is reserved for ~~error~~ denoting no error, we have $2^k - 1$ possible values; this should be more than $n+k$ so that all positions can be acc. for; thus $2^k - 1 > n+k$

$$\text{i.e. } 2^k - k - 1 > n$$

$b_0 \ b_1 \ b_2$

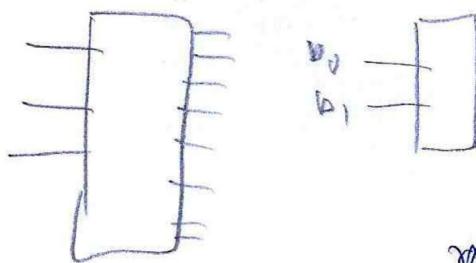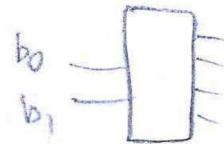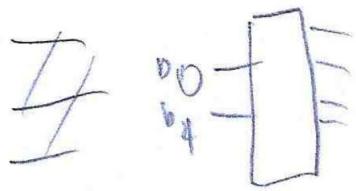

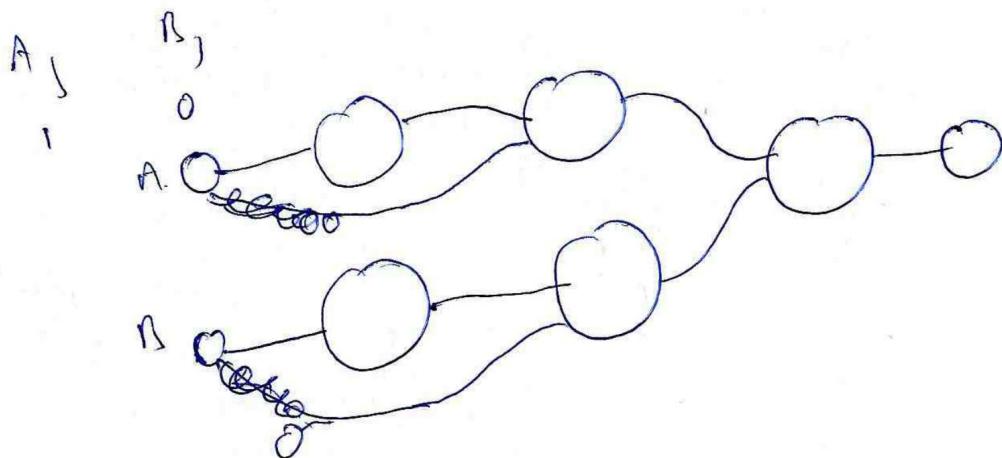
$$\text{reg } A_3 B_3' + n_1 A_2 B_2' + n_1 n_2 A_1 B_1' + n_1 n_2 n_3 A_0 B_0'$$




4. [10 Marks] We wish to design a **3x8 decoder** using **2x4 decoders** as components. Show how to design this using the 2x4 decoders and any additional gates you need. Assume that the 2x4 decoders have 2 input bits and 4 output bits, and implement the usual decoder functionality, with no additional inputs (i.e., no enable, etc.)

inp. - A / B, C

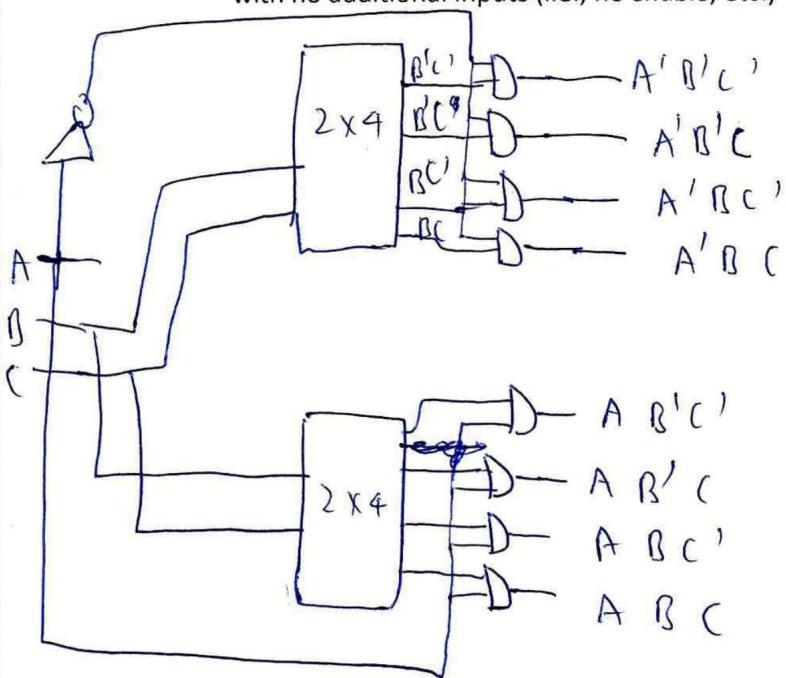

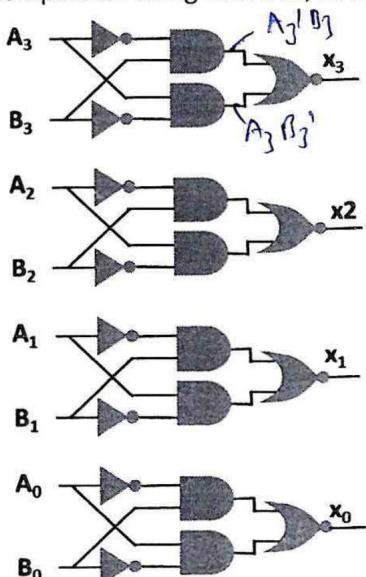5. [10 Marks] Consider the *magnitude comparator* design discussed in class, shown below. Equality between bits can be checked directly with XOR gates. Why do we choose to build the comparator using the AND, INVERTER, etc., instead of just XOR gates? *which take output vars.*



signals separately, which would waste hardware.

$$\Rightarrow C = A_3 B_3' + \bar{A}_3 A_2 B_2' + \bar{A}_3 \bar{A}_2 A_1 B_1' + \bar{A}_3 \bar{A}_2 \bar{A}_1 A_0 B_0'$$

(ass. A_3 before the MSB)
now, in C we need the signals $A_i B_i'$ for all i, similarly for $B > A$ we would need $A_i' B_i$.
using AND, INVERTER etc., we need not find these signals again as they are already present at ~~stage~~. Had we directly used XOR gates,
we would have to find these

0 0 1 0
0 0
0 1 0 1
1 1 1 0 1 0
1 0 0 0 0 0
 0 1 0 1 0

0 0 1 0
0 0 0 0
0 1 0 1
0 1 0 0
1 0 1 0

(Q6)

6. [10 Marks] Let A_0, \dots, A_{n-1} refer to a sequence of n DRAM addresses from which we wish to

access data using the READ operation. Assume that the data accesses can be performed in any order. To optimise performance, what order of addresses should we choose? Justify.


We should reshuffle the addresses so that all the addresses with row address (first r bits) same, come together and are then followed by the next set of addresses with same row address which is bigger than the row address of this set.

e.g. for 2×2 $m=c=2$, if $0010, 0101, 1010, 0000, 0100$, is the seq. & choose $0010, 0000, 0101, 0100, 1010$. This is done as the row decoder output is stored in a row buffer, thus if the next address's row addr. is same it is not decoded again. In our choice, all address with same row address come together, thus the row address needs to be decoded the min. no. of times, which is 1.

 7. [10 Marks] Describe a data structure to represent a combinational gate-level netlist/circuit. You need to ensure that all relevant information is captured in this data structure. Typical operations on this data structure could be: (i) evaluate the outputs for a given set of inputs, or (ii) find the delay through the circuit. Justify your choices. Assume that all gates have one output bit, and one or more input bits.

Data str. - tree. Vertices of the tree will be either leaf nodes or logic gates with children = no. of inputs. The root node is the input signal. A child node has children, value is a and will return a list of signals. The last gate in the netlist (which generally the output) is the root, and each gate is a vertex with children pointing to the gate from which it receives its input. The leaf nodes will be input signals, with their parent equal to the first logic gate they encounter in the tree for evaluating the output. Inputs, and they will contain a list of inputs they require.

While evaluating output, we recursively traverse the tree top to bottom; when we reach a leaf we evaluate output using input list and returns. If we are in a non-child leaf node we take the returns value of the children, evaluate the output and returns. Thus the root is the final answer. To account for delay, we store the delay in each node of that logic gate, then we recursively find max. delay among children, add delay of node, and returns.



$$\begin{aligned}
 A & \leftarrow B, C \\
 P & D \leftarrow A, B, C \\
 E & \leftarrow \text{min}(A, B, C, D)
 \end{aligned}$$

8. [10 Marks] Given a set of concurrent VHDL signal assignment statements that are triggered (scheduled for execution) at the same time, in what order should we execute them in the simulator? Give the strategy and justify.

Let the triggering signals be n_1, n_2, \dots

first we execute those stat. which edge whose RHS depends only on n_1, n_2, \dots i.e they are of form $y_i \leftarrow 1(n_1, n_2, \dots)$. Then we execute those stat. whose RHS depends on \oplus the peer.


signals LHS having input signals only i.e $y_2 \leftarrow 1(y_1, n_1, \dots)$. The strategy maintain a list, whose initial val. are triggering signals. Then search for stat. whose RHS depends on signals in this list. As for each such stat., evaluate RHS and add LHS to the list, \oplus and start value of RHS. then repeat the same process with this new list, till all stat. have been evaluated. (When we evaluate a stat., we delete it from the list of stat. to be searched)

This is correct, as to evaluate a expr. of signals, we need to know value of each signal beforehand. So first we only those stat. can be eval. whose RHS depends only on triggering signals, then those whose RHS depends on the \oplus triggering and the prev. stat. RHS, and so on. (since now we know value of peer stat. RHS)

9. [10 Marks] In our Finite State Machine discussion, we argued that FSM states can be symbolic (S0, S1, etc., instead of 00, 01, etc.) What is the advantage of starting with symbolic states in the FSM? If the states are symbolic, it becomes easier to perform state redctn. Also, it may happen that after state redctn, the no. of flip flops required decreases. If we had initially chosen n flip flops and assigned states, and the no. of states reduces after state red. s.t we now require lesser no. of flip flops, then we will have to reassign states to acc. for that. This problem is not faced for symbolic states, where we assign states after state red. and hence find no. off at the end.

Also, after redⁿ, we can also see which state encoding gives us simpler logic circuitry; this is not possible if we assign states in the beginning.



A	B	C	D
0	0	0	0
0	1	1	0
1	0	0	1
1	1	1	1

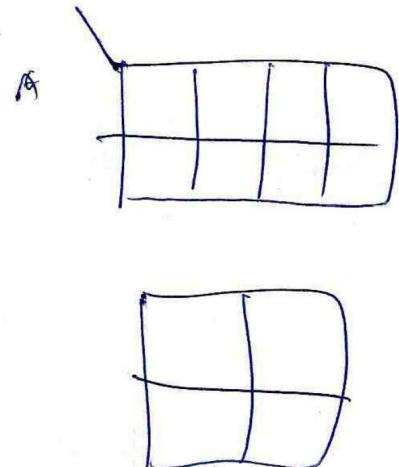

~~ABR ABR~~

A	B	$A \oplus B$	C	D
0	0	0	0	0
0	1	1	1	0
1	0	1	0	1
1	1	0	1	1

$$C = A \oplus A \oplus B$$

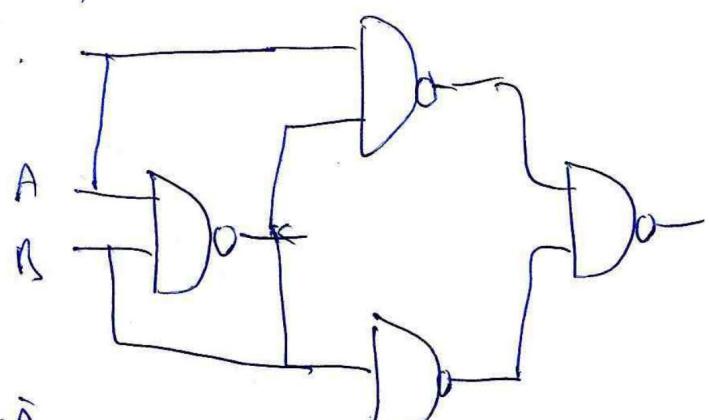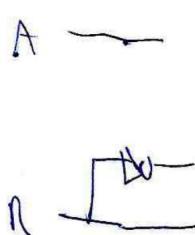


$$\begin{aligned}
 & A \oplus B = (\bar{A} + \bar{B}) + \bar{A} \\
 & = A \cdot B + \bar{A} = \overline{\bar{A} \cdot \bar{A} + B} \\
 & = \overline{(A \cdot \bar{B})}
 \end{aligned}$$

10. [10 Marks] Is the State Reduction step guaranteed to reduce the size of the final generated netlist? Why?


~~Ans: No, this step is not guaranteed to reduce the size of the final generated netlist. There are two factors - redⁿ in no. of flip flops, and Boolean 1ⁿ complexity of the output and input egⁿ of flip flop.~~ It is not necessary that state redⁿ leads to \downarrow in no. of FF. Even if it does, the complexity of the Boolean 1ⁿ of outputs and inputs of FF may easily increase. ~~thus even if the incr. in no. of logic gates, for Boot. 1ⁿ of outputs and inputs~~ uncompensate the redⁿ in no. of FF, the netlist size can increase. Also, it's poss. that no. of FF doesn't \downarrow , but complexity of Boolean 1ⁿ \uparrow ; thus netlist size can increase also in this step.

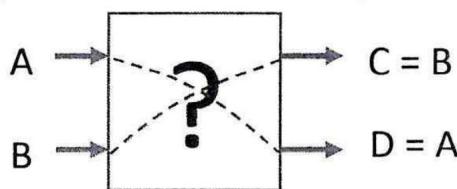11. [15 Marks] Draw a combinational circuit to complete the following picture, where the order of input signals A and B, is reversed in the outputs, the condition being that **no two wires should cross each other**. You are allowed to use only the following gates: INVERTER, NAND, NOR, AND, OR. Assume that no wire crossings occur within the gates. [Hint: Consider an application of the XOR function. Remember that using XOR gate directly is not allowed.]



$$C = A \oplus (A \oplus B)$$

$$D = B \oplus A \oplus B$$

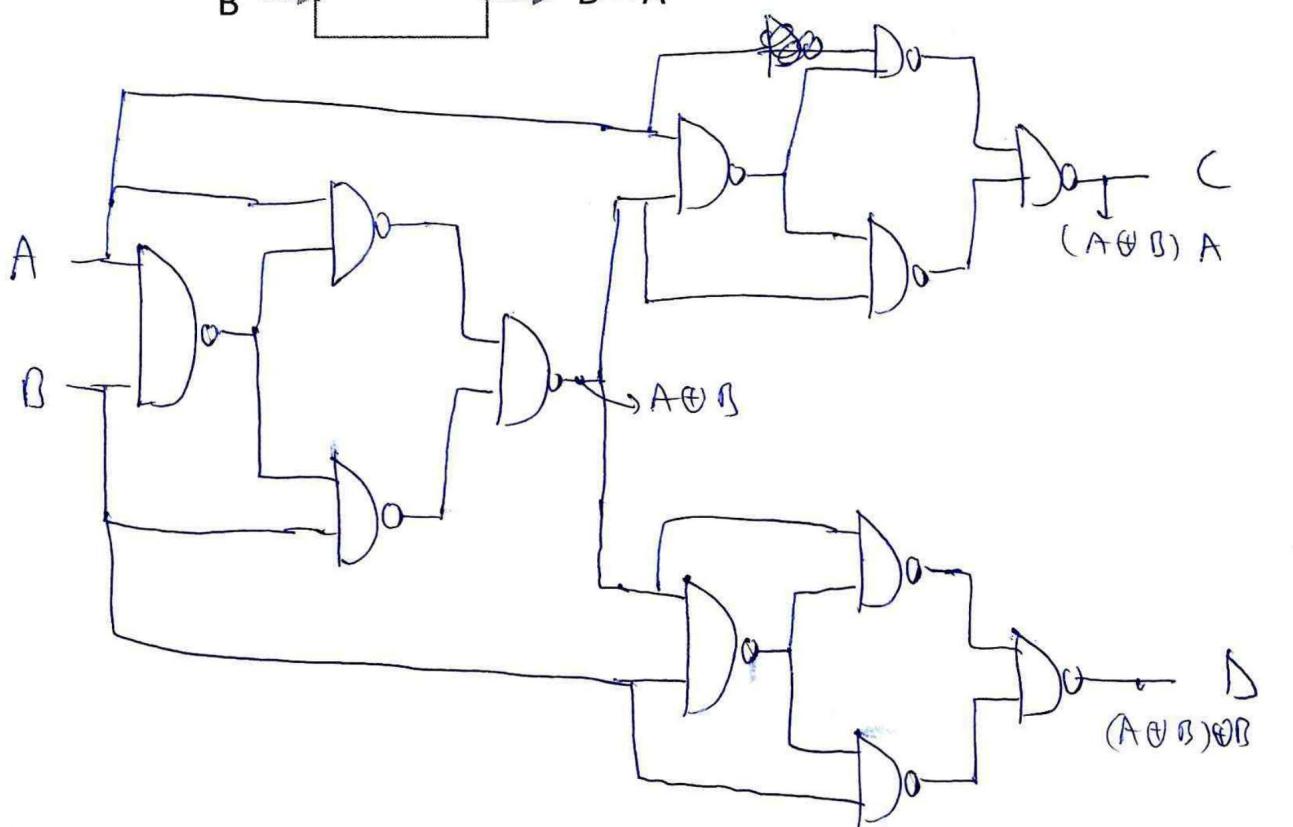

$$\text{from TT, } C = (A \oplus B) \oplus A$$

$$D = (A \oplus B) \oplus B$$

